



## 3-bit Arithmetic and Logic Unit (ALU)

Name	ID
Aya Oraby	201900967
Nada Ghafagy	202001944
Menna Khaled	202301665

Designing and implement a 4-bit Arithmetic and Logic Unit (ALU) that has inputs A & B to do the following:

Operation	Output (E)
OR	$E = A \vee B$
AND	$E = A \wedge B$
CMP	$E = B'$
ADD	$E = A + B$
SUB	$E = A - B$
XOR	$E = A \oplus B$
Two's CMP	$A' + 1$
INC	$E = B + 1$

To make that

All the operation will be connected to 8:1 Multiplexer and the selector choose what operation should be done

Truth table of Multiplexer 8:1

S1	S2	S3	Out
0	0	0	AB (AND)
0	0	1	$A \vee B$ (OR)
0	1	0	$A \wedge B$ (XOR)
0	1	1	$\sim B$ (CMP)
1	0	0	$A + B$ (ADD)
1	0	1	$A - B$ (SUB)
1	1	0	ASR (A3A2A1)
1	1	1	INC (B+1)


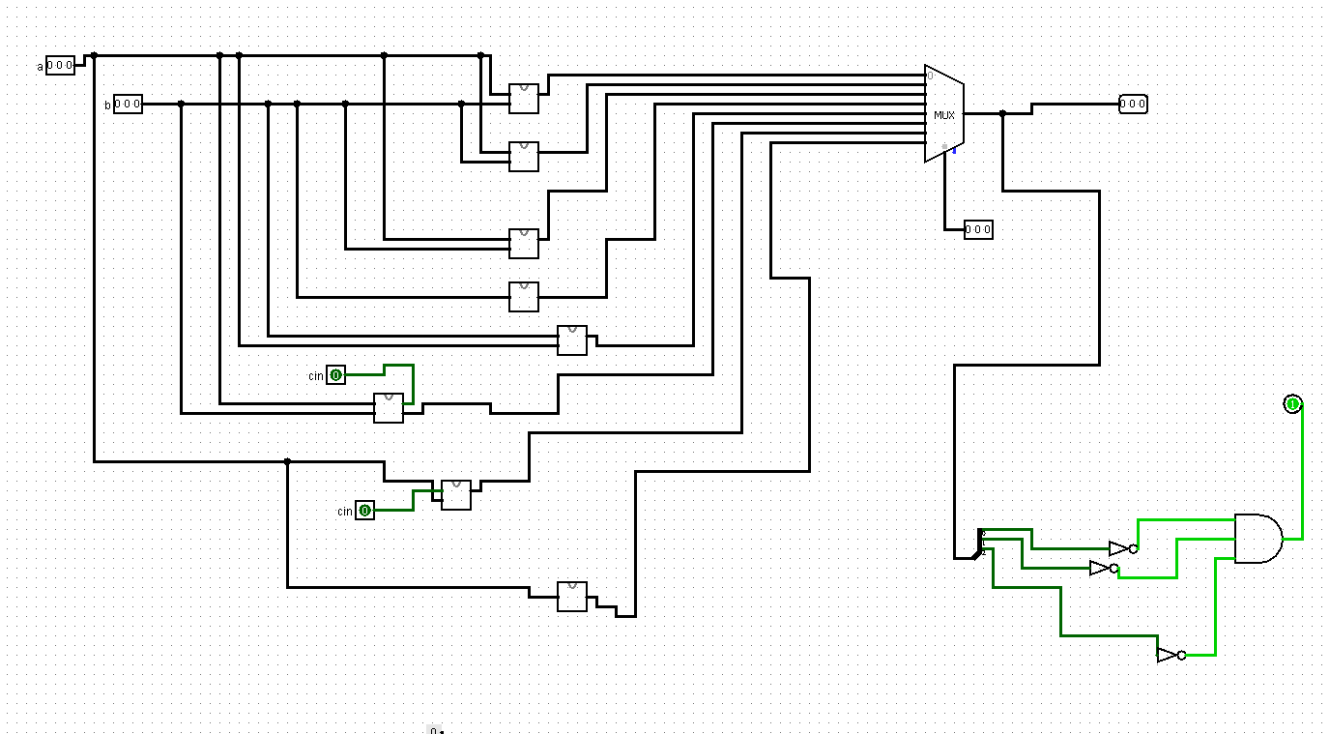


Figure 1 Multiplexer 8:1

## AND GATE

Both A and B are 4 bits so all the output of AND GATE is

A	B	OUT
0	0	0
0	1	0
1	0	0
1	1	1

 

```
module AND_GATE (  
    input logic [2:0] a, b,  
    output logic [2:0] c  
);  
    assign c = a & b;  
endmodule
```

Figure 3 AND Gate using System Verilog

## OR GATE

Both A and B are 4 bits so all the output of OR GATE is

A	B	OUT
0	0	0
0	1	1
1	0	1
1	1	1

 


Figure 4ORGate

```
module OR_GATE (  
    input logic [2:0] a, b,  
    output logic [2:0] c  
);  
    assign c = a | b;  
endmodule
```

Figure 5ORGate Using SyestemVerilog

## XOR Gate

Both A and B are 4 bits so all the output of XOR GATE is

A	B	OUT
0	0	0
0	1	1
1	0	1
1	1	1

 


Figure 6XOR GATE

```
module XOR_GATE (  
    input logic [2:0] a, b,  
    output logic [2:0] c  
);  
    assign c = a ^ b;  
endmodule
```

Figure 7XOR GATE Using System Verilog

## CMP Gate

Complement Truth Table is

B	~B
1	0
0	1

 


Figure 8 NOT Gate

```
module CMP_GATE (  
    input logic [2:0] b,  
    output logic [2:0] c  
);  
    assign c = ~b;  
endmodule
```

Figure 9 CMP USING System Verilog

To be able to Add four bit A,B we must have 4-bit full adder

The design I choose is two half adder that makes Full Adder  
and when connect 4 Full Adder then we make 4 bit Full Adder

### Half Adder

 


Figure 10HalfAdder

```
module halfadder (input a,b  
,output sum ,carry);  
sum = a^b ;  
carry = a&b ;  
endmodule
```

Figure 11HalfAdder Using SystemVerilog

Truth Table			
Input		Output	
A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1



WE Connect two half adder to make fulladder

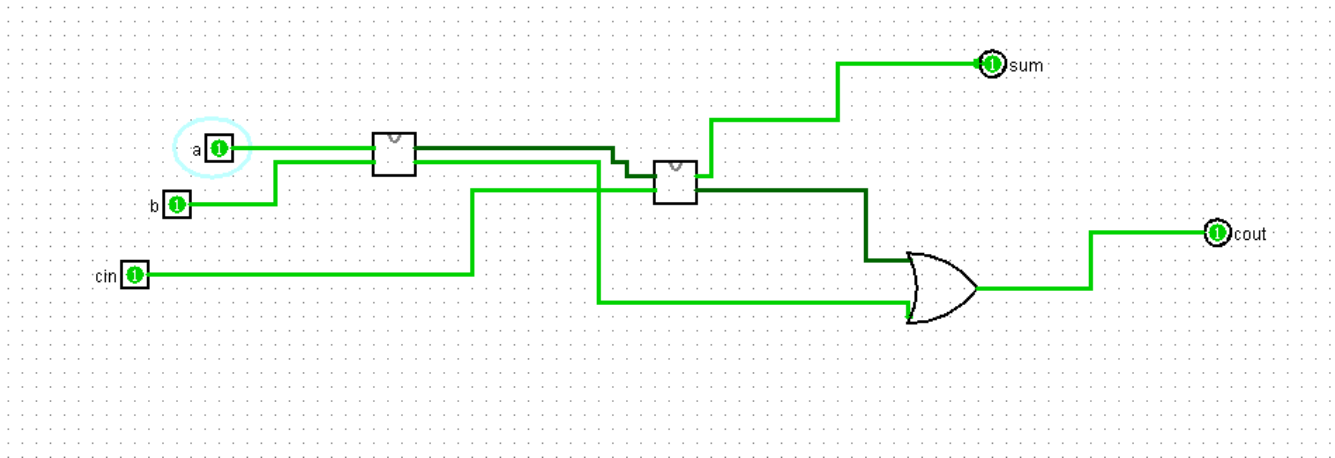


Figure 12FullAddrCircuit

Full Adder Truth table

INPUTS			OUTPUTS	
A	B	C <sub>in</sub>	SUM	CARRY <sub>OUT</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

```

module full_adder (
    input logic a, b, cin,
    output logic sum, cout
);
    logic p, g;


    // Propagate and generate signals
    assign p = a ^ b;      // p = a XOR b
    assign g = a & b;      // a AND b

    // Sum and carryout
    assign sum = p ^ cin;  // sum = (a XOR b) XOR cin
    assign cout = g | (p & cin); // Carryout cout = g OR (p AND cin)
endmodule

```

Figure 14 4-bitFullAdder

 We connect 4 full adder to make 4-bit full Adder



## ADD Gate

Based on full Adder

output = A+B


 


Figure 15 ADD Gate

```
module ADD_GATE (  
    input logic [2:0] a, b,  
    output logic [2:0] sum,  
    output logic cout, v  
);  
    logic c1, c2;  
    full_adder add1 (a[0], b[0], 0, sum[0], c1);  
    full_adder add2 (a[1], b[1], c1, sum[1], c2);  
    full_adder add3 (a[2], b[2], c2, sum[2], cout);  
  
    // Overflow detection using XOR  
    assign v = c2 ^ cout; // overflow occurs when tl  
endmodule
```

Figure 16 ADD Using System Verilog

## SUB Gate

 

The Operation Of Subtraction is  $A - B$

So it can be done by  $A + \sim B + 1$

The reason this works is because in two's complement representation, negating a number (finding its two's complement) involves inverting all the bits and then adding 1. This is a convenient property that allows subtraction to be performed using addition.

So

$$A - B = A + \sim B + 1$$

```

module SUB_GATE (
    input logic [2:0] a, b,
    output logic [2:0] diff,
    output logic cout, v
);
    logic c1, c2;
    full_adder sub1 (a[0], ~b[0], 1, diff[0], c1);
    full_adder sub2 (a[1], ~b[1], c1, diff[1], c2);
    full_adder sub3 (a[2], ~b[2], c2, diff[2], cout);

    // Overflow detection using XOR
    assign v = c2 ^ cout; // overflow occurs when th
endmodule

```

Figure 17 SUB using System Verilog

## INCREMENT OPERATION

B+1 so A is constant with zero value using 4-bit full-adder

0+B+1

 


Figure 18 Increment Operation

```


module INC_GATE (
    input logic [2:0] b,
    output logic [2:0] sum
);
    logic c1, c2, cout;
    full_adder F1 (0, b[0], 1, sum[0], c1);
    full_adder F2 (0, b[1], c1, sum[1], c2);
    full_adder F3 (0, b[2], c2, sum[2], cout);
endmodule

```

Figure 19 Increment Using System Verilog

Two's complement

Invert the number then adding one

 

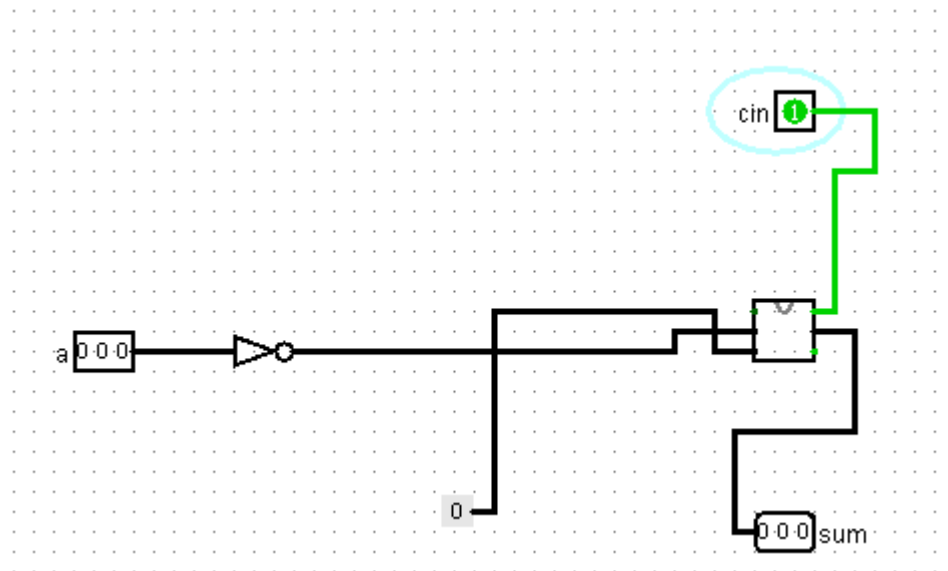


Figure 20 Two's complement Operation

```


module TWOS_COMP_GATE (
    input logic [2:0] a,
    output logic [2:0] y
);
    logic [2:0] not_a;
    logic c1, c2, cout;
    full_adder add1 (~a[0], 0, 1, y[0], c1);
    full_adder add2 (~a[1], 0, c1, y[1], c2);
    full_adder add3 (~a[2], 0, c2, y[2], cout);
endmodule

```


Figure 21 Two's complement using systemverilog
 
## OverFlow

Overflow Occurs when  $C_{in} \neq C_{out}$ . The above expression for overflow can be explained below Analysis.



 
To check the overflow  
overflow occurs when the carry into the MSB and the carry out differ



Output  
0.

bit Z, where  $Z = 1$  if  $E =$



 

We take the output of multiplexer and connect it with inverter gate  
so when the output is 000 so the output of And gate after not gate is zero so  
Z =

```
module ALU (  
    input logic [2:0] A, B,  
    output logic z, v,  
    output logic [2:0] result,  
    input logic [2:0] select  
);  
    logic [2:0] And, Or, X_or, cmpgatee, addd, subb, incc, twos_comp;  
    logic cout;  
  
    AU au (A, B, addd, subb, incc, twos_comp, cout, v);  
    LU lu (A, B, And, Or, X_or, cmpgatee);  
    mux8 mux8_ALU (And, Or, X_or, cmpgatee, addd, subb, incc, twos_comp, select, result);  
    assign z = ~result[0] & ~result[1] & ~result[2]; // Zero flag  
endmodule
```

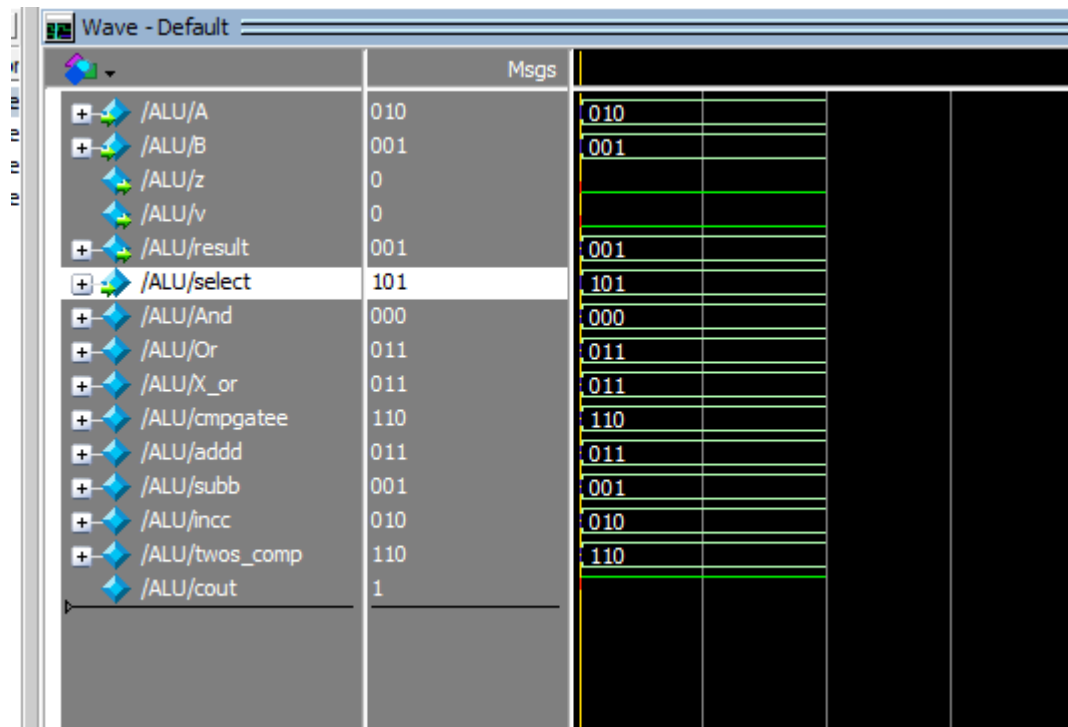


Figure 22 suimulation of ALU

The result is 001 as the gate is Subtraction 101

so

$$010 - 001 = 001$$